

5.41 Name the components shown here.

(a)



(b)



(c)



(d)



(e)



ANSWERS

- 5.30 (h) 1.8 kΩ ± 90 Ω
- 5.30 (i) 2.2 kΩ ± 110 Ω
- 5.30 (j) 1 MΩ ± 50 kΩ
- 5.31 1k0+680R+270R+82R+27R = 2259 Ω
- 5.32 390R+120R+330R+68R+47R = 955 Ω
- 5.33 10k+3k3+18k+1k2+2k2 = 34.7 kΩ
- 5.34 3k3//3k3//2k2//2k2 = 660 Ω
- 5.35 1k2//5k6//1k2//5k6 = 494 Ω
- 5.36 68k//82k//120k//270k = 25.7 kΩ
- 5.37 12R+100R//(18R+82R) = 62 Ω
- 5.38 220R+680R//(220R+220R+220R) = 357 Ω
- 5.39 18R//(12R+470R//(220R+220R)+12R) = 16.8 Ω
- 5.40 56k//(10R+3k3//(470R+2k7+820R)+10R) = 3.71 kΩ
- 5.41 (a) slide potentiometer, (b) wire-wound pot, (c) rotary potentiometer, (d) carbon-compound resistor, (e) variac (MOV or VDR).

- 5.30 (a) 10 Ω ± 1 Ω
- 5.30 (b) 56 kΩ ± 2800 Ω
- 5.30 (c) 3.3 kΩ ± 165 Ω
- 5.30 (d) 470 kΩ ± 23.5 kΩ
- 5.30 (e) 680 Ω ± 68 Ω
- 5.30 (f) 2.7 kΩ ± 135 Ω
- 5.30 (g) 820 Ω ± 41 Ω
- 5.27 221 V
- 5.26 124.6°C, 125.3°C, 123.4°C
- 5.25 25.5 Ω
- 5.24 25.5 Ω
- 5.23 2.84E-8 Ωm
- 5.22 58.1 m
- 5.21 688 Ω (688 mΩ)

Sample pages